



# 250P: Computer Systems Architecture

## Lecture 2: Basics of Digital Design

Anton Burtsev  
September, 2021
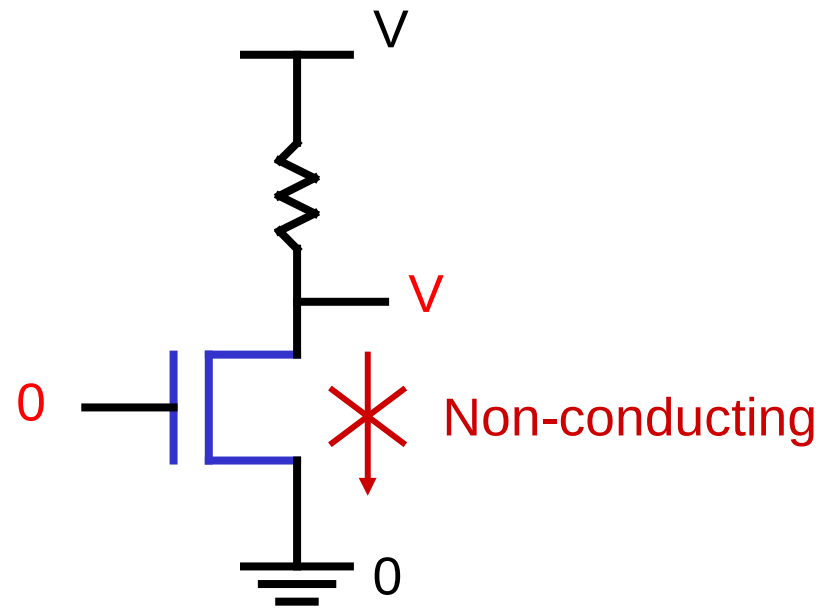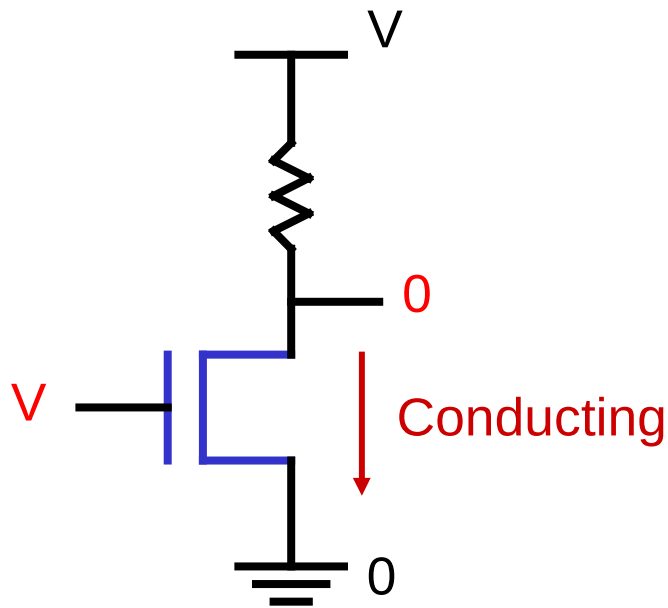
# Digital Design Basics

- Two voltage levels – high and low (1 and 0, true and false)  
Hence, the use of binary arithmetic/logic in all computers
- A transistor is a 3-terminal device that acts as a switch



# Logic Blocks

- A logic block has a number of binary inputs and produces a number of binary outputs – the simplest logic block is composed of a few transistors
- A logic block is termed *combinational* if the output is only a function of the inputs
- A logic block is termed *sequential* if the block has some internal memory (state) that also influences the output
- A basic logic block is termed a *gate* (AND, OR, NOT, etc.)

We will only deal with combinational circuits today

# Truth Table

- A truth table defines the outputs of a logic block for each set of inputs
- Consider a block with 3 inputs A, B, C and an output E that is true only if *exactly* 2 inputs are true

A	B	C	E

# Truth Table

- A truth table defines the outputs of a logic block for each set of inputs
- Consider a block with 3 inputs A, B, C and an output E that is true only if *exactly* 2 inputs are true

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Can be compressed by only representing cases that have an output of 1

# Boolean Algebra

- Equations involving two values and three primary operators:
  - OR : symbol  $+$  ,  $X = A + B \rightarrow X$  is true if at least one of A or B is true
  - AND : symbol  $\cdot$  ,  $X = A \cdot B \rightarrow X$  is true if both A and B are true
  - NOT : symbol  $\bar{\quad}$  ,  $X = \bar{A} \rightarrow X$  is the inverted value of A

# Boolean Algebra Rules

- Identity law :  $A + 0 = A$  ;  $A \cdot 1 = A$
- Zero and One laws :  $A + 1 = 1$  ;  $A \cdot 0 = 0$
- Inverse laws :  $A \cdot \overline{A} = 0$  ;  $A + \overline{A} = 1$
- Commutative laws :  $A + B = B + A$  ;  $A \cdot B = B \cdot A$
- Associative laws :  $A + (B + C) = (A + B) + C$   
 $A \cdot (B \cdot C) = (A \cdot B) \cdot C$
- Distributive laws :  $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$   
 $A + (B \cdot C) = (A + B) \cdot (A + C)$

# DeMorgan's Laws

- $\overline{A + B} = \overline{A} \cdot \overline{B}$

- $\overline{A \cdot B} = \overline{A} + \overline{B}$

- Confirm that these are indeed true



# Logic for common arithmetic operations

## Simple ALU

# Pictorial Representations


AND



OR




NOT

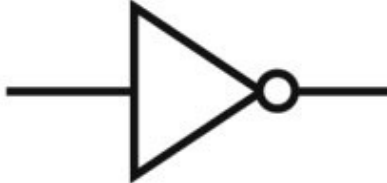

Source: H&P textbook

What logic function is this?

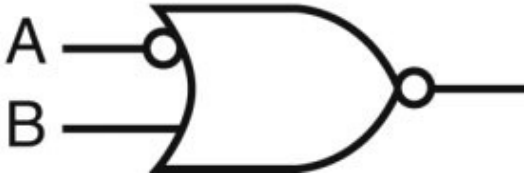

Source: H&P textbook

# Boolean Equation

- Consider the logic block that has an output E that is true only if exactly two of the three inputs A, B, C are true

Multiple correct equations:

Two must be true, but all three cannot be true:

$$E = ((A \cdot B) + (B \cdot C) + (A \cdot C)) \cdot \overline{(A \cdot B \cdot C)}$$

Identify the three cases where it is true:

$$E = (A \cdot B \cdot \overline{C}) + (A \cdot C \cdot \overline{B}) + (C \cdot B \cdot \overline{A})$$

# Sum of Products

- Can represent any logic block with the AND, OR, NOT operators
  - Draw the truth table
  - For each true output, represent the corresponding inputs as a product
  - The final equation is a sum of these products

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$(A \cdot B \cdot \overline{C}) + (A \cdot C \cdot \overline{B}) + (C \cdot B \cdot \overline{A})$$

- Can also use “product of sums”
- Any equation can be implemented with an array of ANDs, followed by an array of ORs


# NAND and NOR

- NAND : NOT of AND :  $A \text{ nand } B = \overline{A \cdot B}$
- NOR : NOT of OR :  $A \text{ nor } B = \overline{A + B}$
- NAND and NOR are *universal gates*, i.e., they can be used to construct any complex logical function

# Common Logic Blocks – Decoder


Takes in N inputs and activates one of  $2^N$  outputs

$I_0$	$I_1$	$I_2$	$O_0$	$O_1$	$O_2$	$O_3$	$O_4$	$O_5$	$O_6$	$O_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

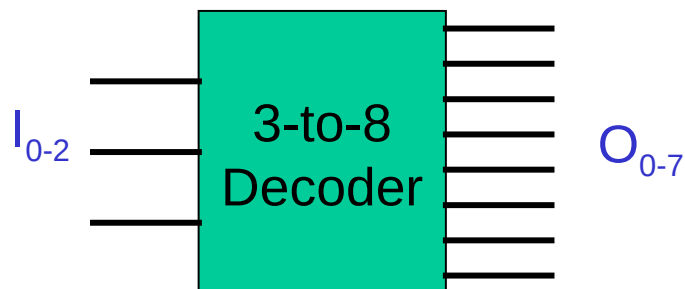
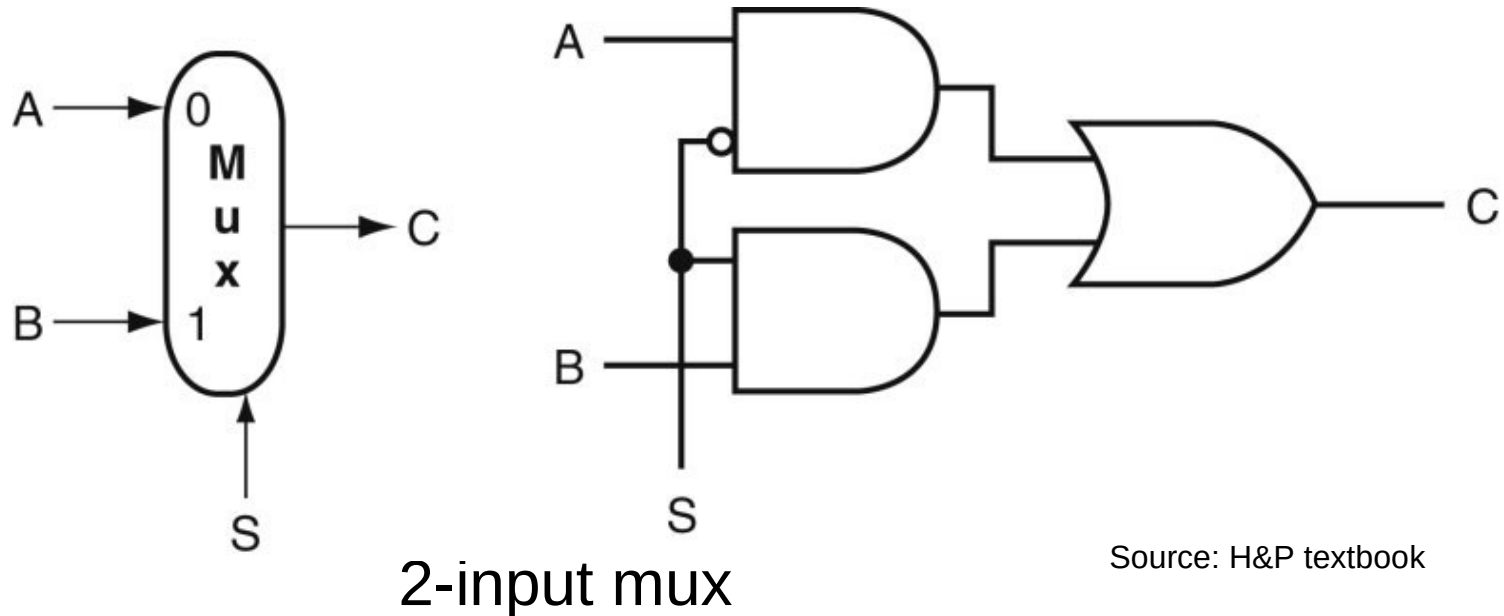
# Common Logic Blocks – Multiplexor

- Multiplexor or selector: one of N inputs is reflected on the output depending on the value of the  $\log_2 N$  selector bits



# Adder Algorithm

	1	0	0	1
	0	1	0	1
Sum	1	1	1	0
Carry	0	0	0	1

Truth Table for the above operations:

A	B	Cin	Sum	Cout
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		



# Adder Algorithm

	1	0	0	1
	0	1	0	1
Sum	1	1	1	0
Carry	0	0	0	1

Truth Table for the above operations:


A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Equations:

$$\begin{aligned} \text{Sum} = & \text{Cin} \cdot \overline{A} \cdot \overline{B} + \\ & B \cdot \overline{\text{Cin}} \cdot \overline{A} + \\ & A \cdot \overline{\text{Cin}} \cdot \overline{B} + \\ & A \cdot B \cdot \text{Cin} \end{aligned}$$

$$\begin{aligned} \text{Cout} = & A \cdot B \cdot \text{Cin} + \\ & A \cdot B \cdot \overline{\text{Cin}} + \\ & A \cdot \text{Cin} \cdot \overline{B} + \\ & B \cdot \text{Cin} \cdot \overline{A} \\ = & A \cdot B + \\ & A \cdot \text{Cin} + \\ & B \cdot \text{Cin} \end{aligned}$$

# Carry Out Logic

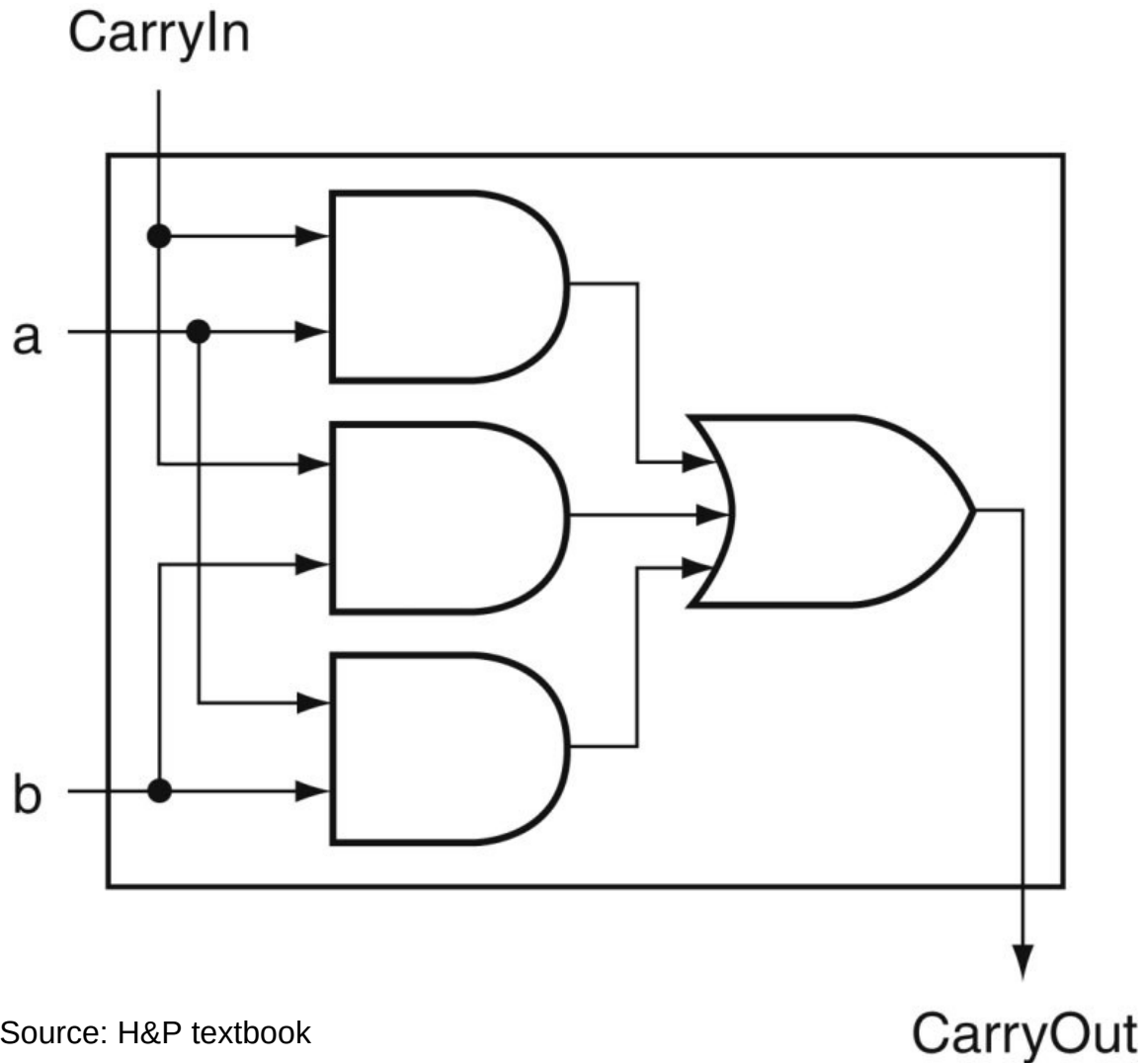

Equations:


$$\begin{aligned} \text{Sum} = & \text{Cin} \cdot \overline{A} \cdot \overline{B} + \\ & B \cdot \overline{\text{Cin}} \cdot \overline{A} + \\ & A \cdot \overline{\text{Cin}} \cdot \overline{B} + \\ & A \cdot B \cdot \text{Cin} \end{aligned}$$

$$\begin{aligned} \text{Cout} = & A \cdot B \cdot \text{Cin} + \\ & A \cdot B \cdot \overline{\text{Cin}} + \\ & A \cdot \text{Cin} \cdot \overline{B} + \\ & B \cdot \text{Cin} \cdot \overline{A} \\ = & A \cdot B + \\ & A \cdot \text{Cin} + \\ & B \cdot \text{Cin} \end{aligned}$$

Source: H&P textbook

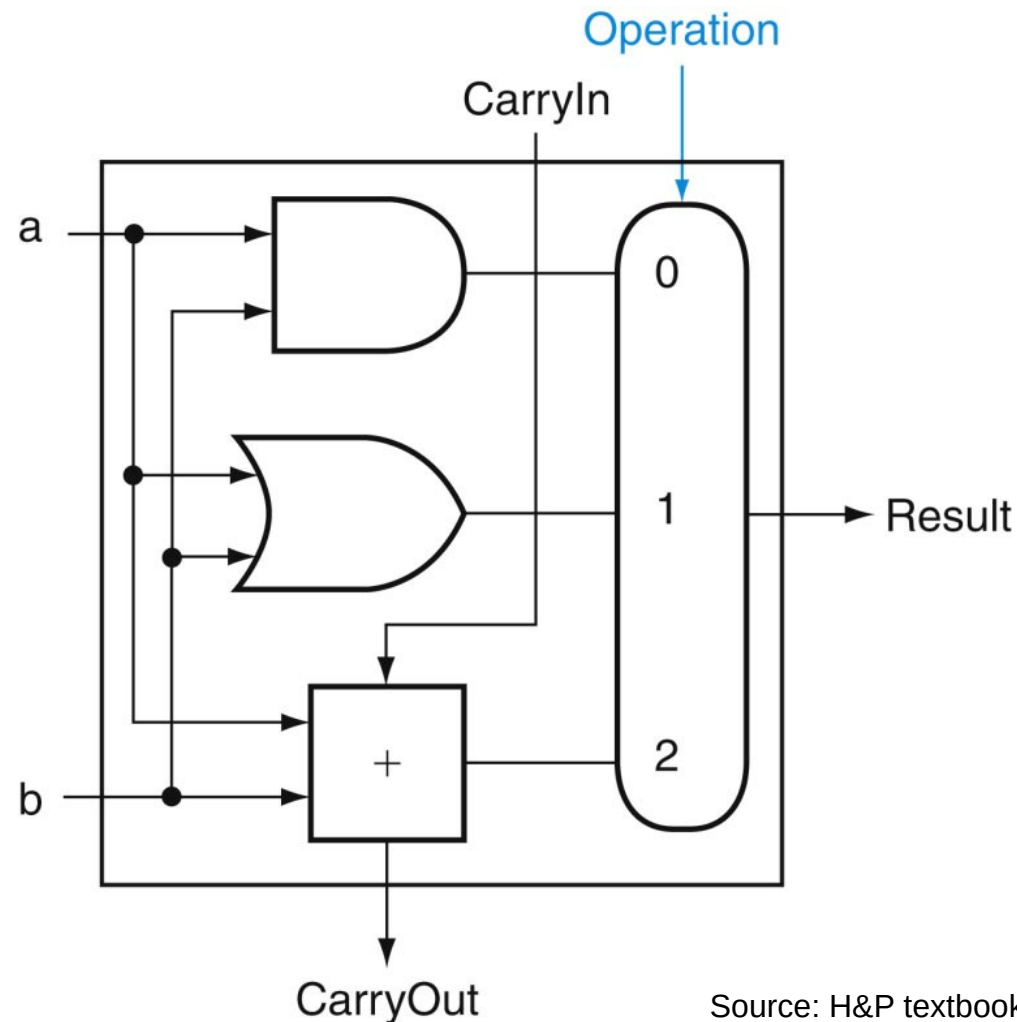
# 1-Bit ALU with Add, Or, And

- Multiplexor selects between Add, Or, And operations


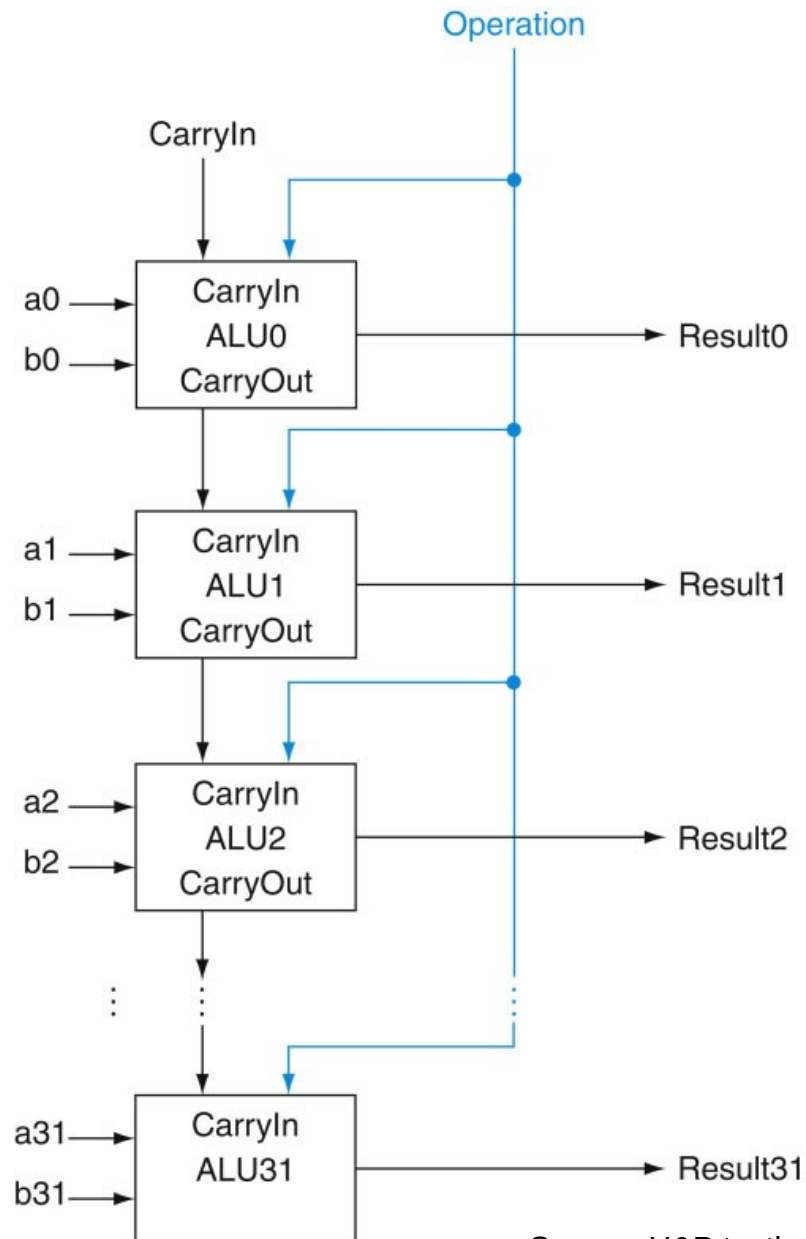
# 32-bit Ripple Carry Adder


1-bit ALUs are connected “in series” with the carry-out of 1 box going into the carry-in of the next box


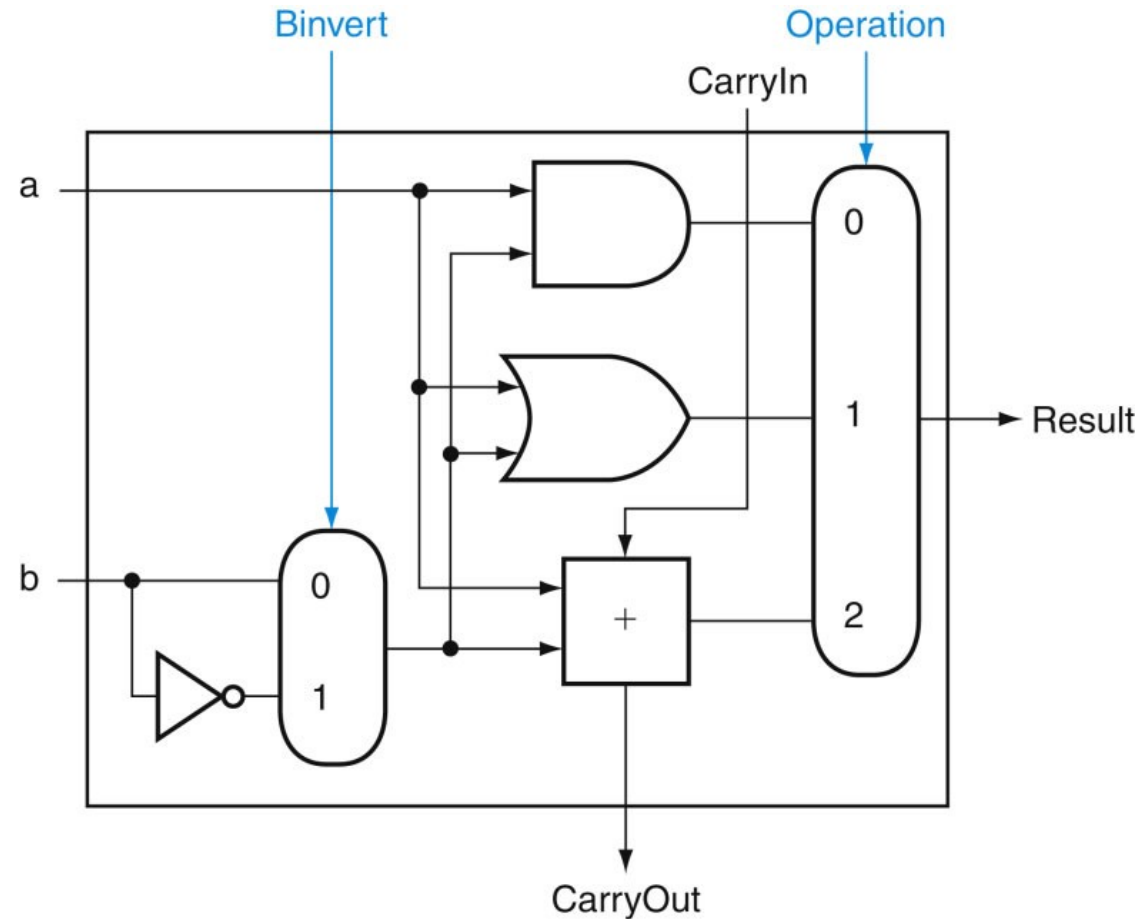
# Incorporating Subtraction


Must invert bits of B and add a 1

- Include an inverter
- CarryIn for the first bit is 1
- The CarryIn signal (for the first bit) can be the same as the Binvert signal




Source: H&P textbook

# Incorporating NOR and NAND

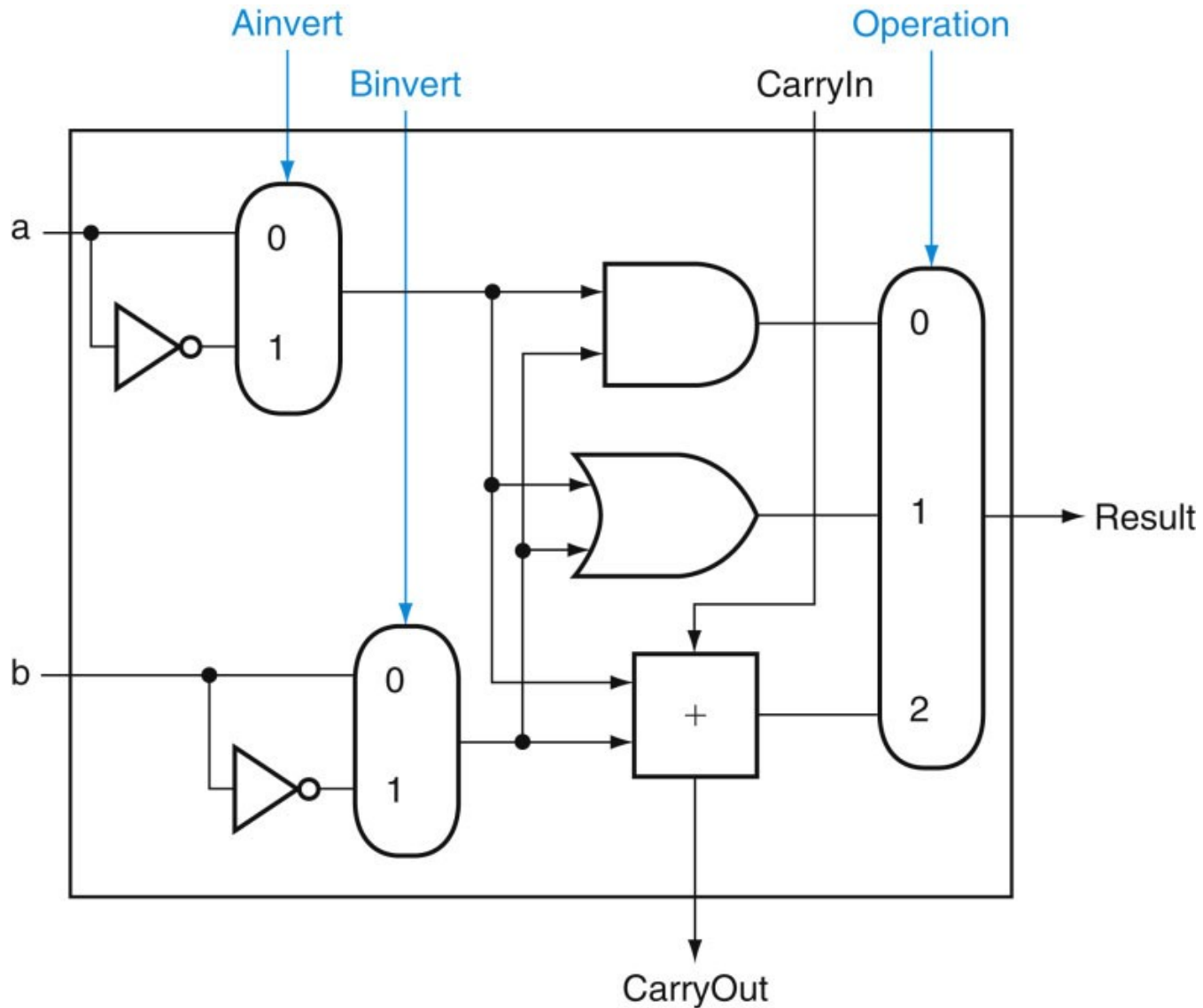

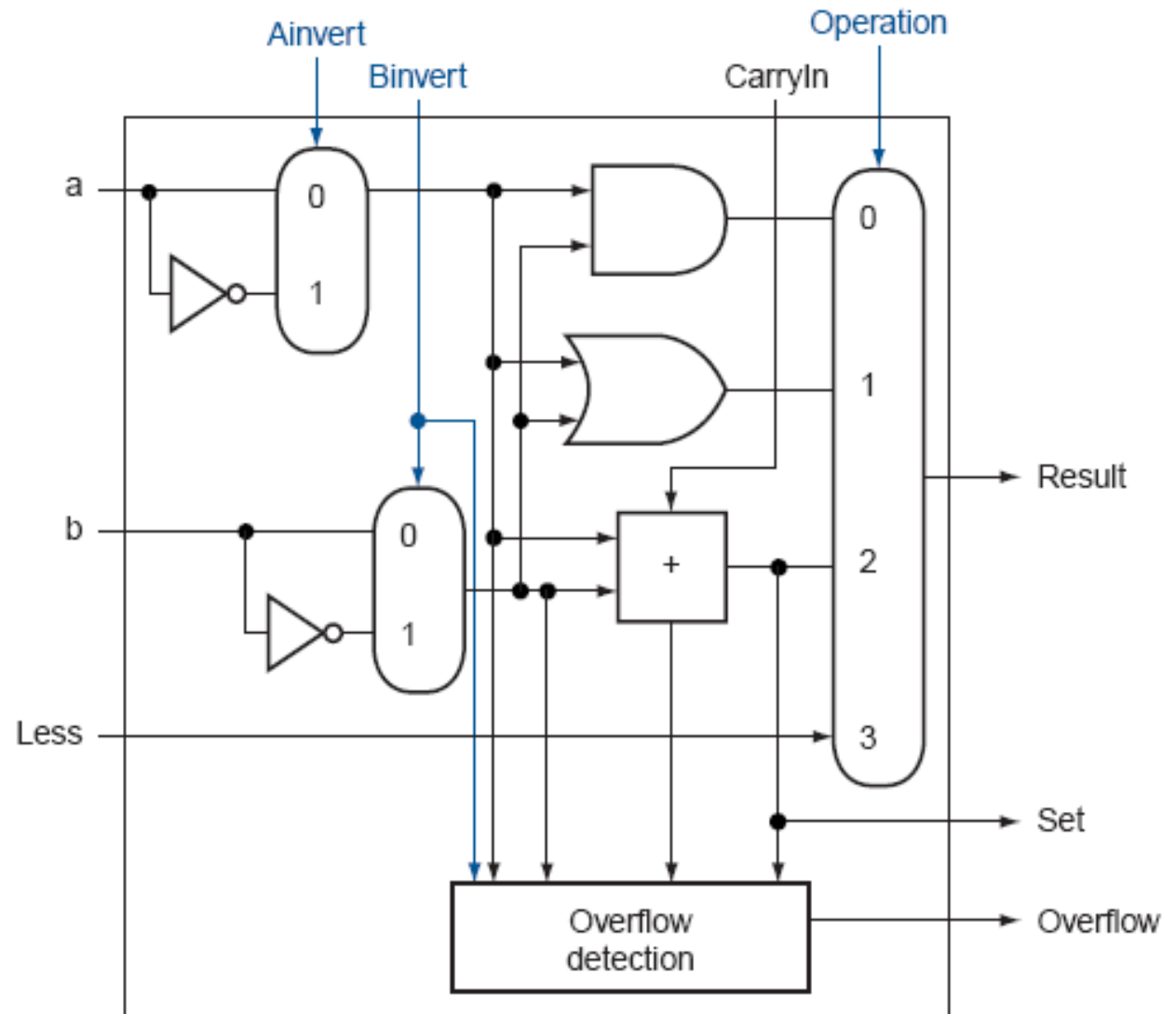
# Incorporating cmp (set bit when less than)

- Perform  $a - b$  and check the sign
- New signal (Less) that is zero for ALU boxes 1-31
- The 31<sup>st</sup> box has a unit to detect overflow and sign – the sign bit serves as the Less signal for the 0<sup>th</sup> box


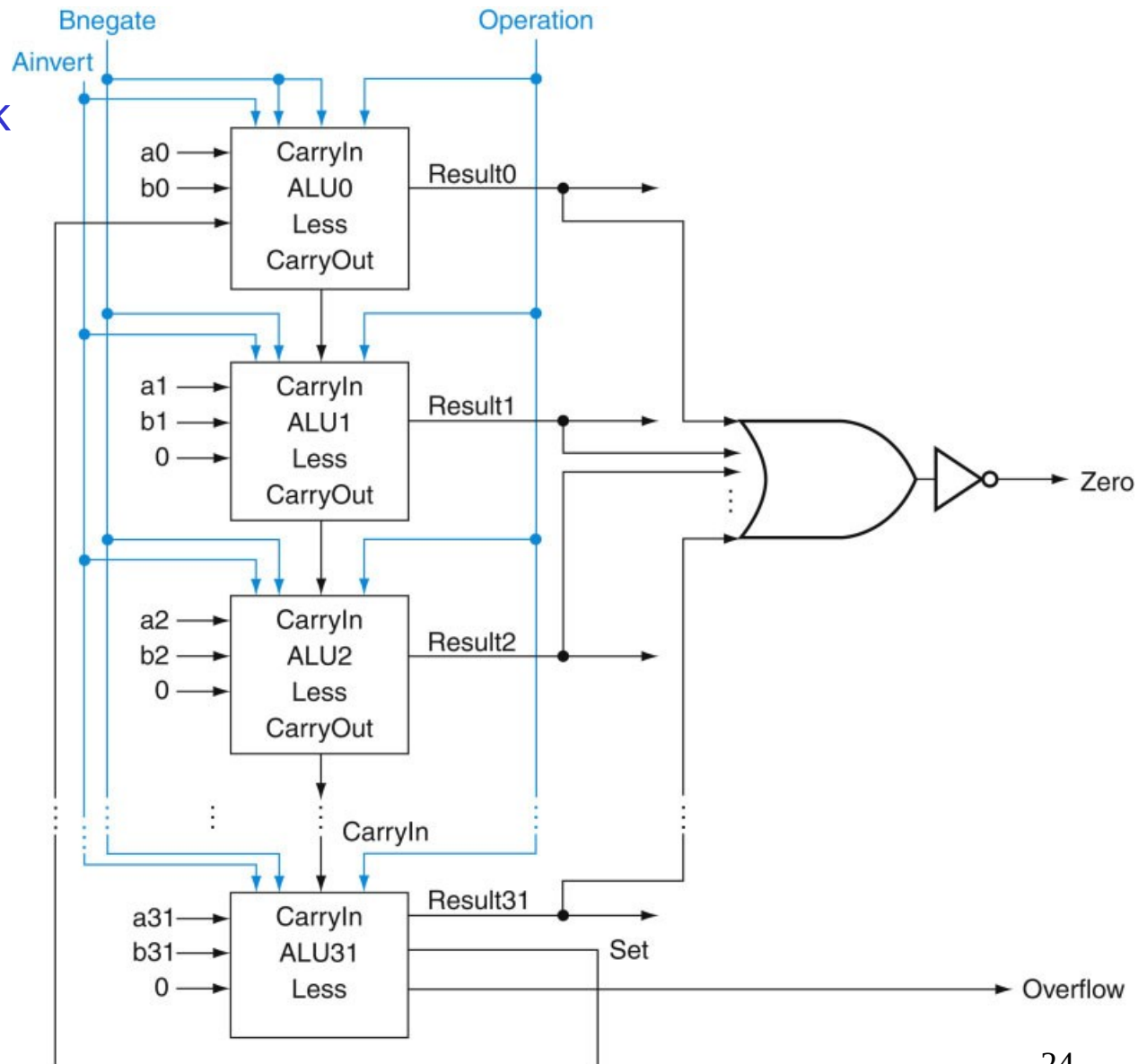
# Incorporating cmp (set bit when less than)


- Perform  $a - b$  and check the sign
- New signal (Less) that is zero for ALU boxes 1-31
- The 31<sup>st</sup> box has a unit to detect overflow and sign – the sign bit serves as the Less signal for the 0<sup>th</sup> box





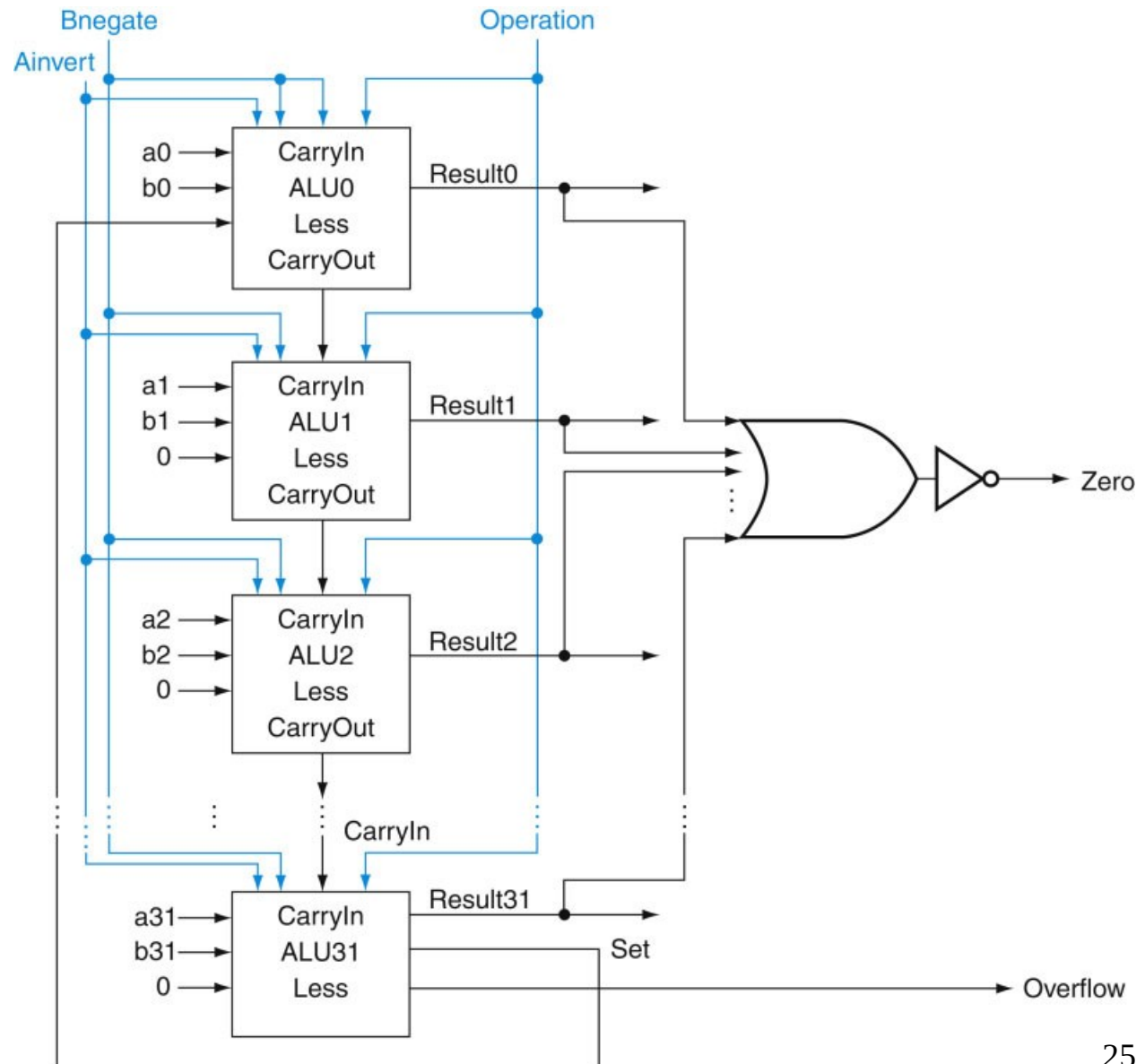
# Incorporating jeq (jump when equal)

- Perform  $a - b$  and confirm that the result is all zero's


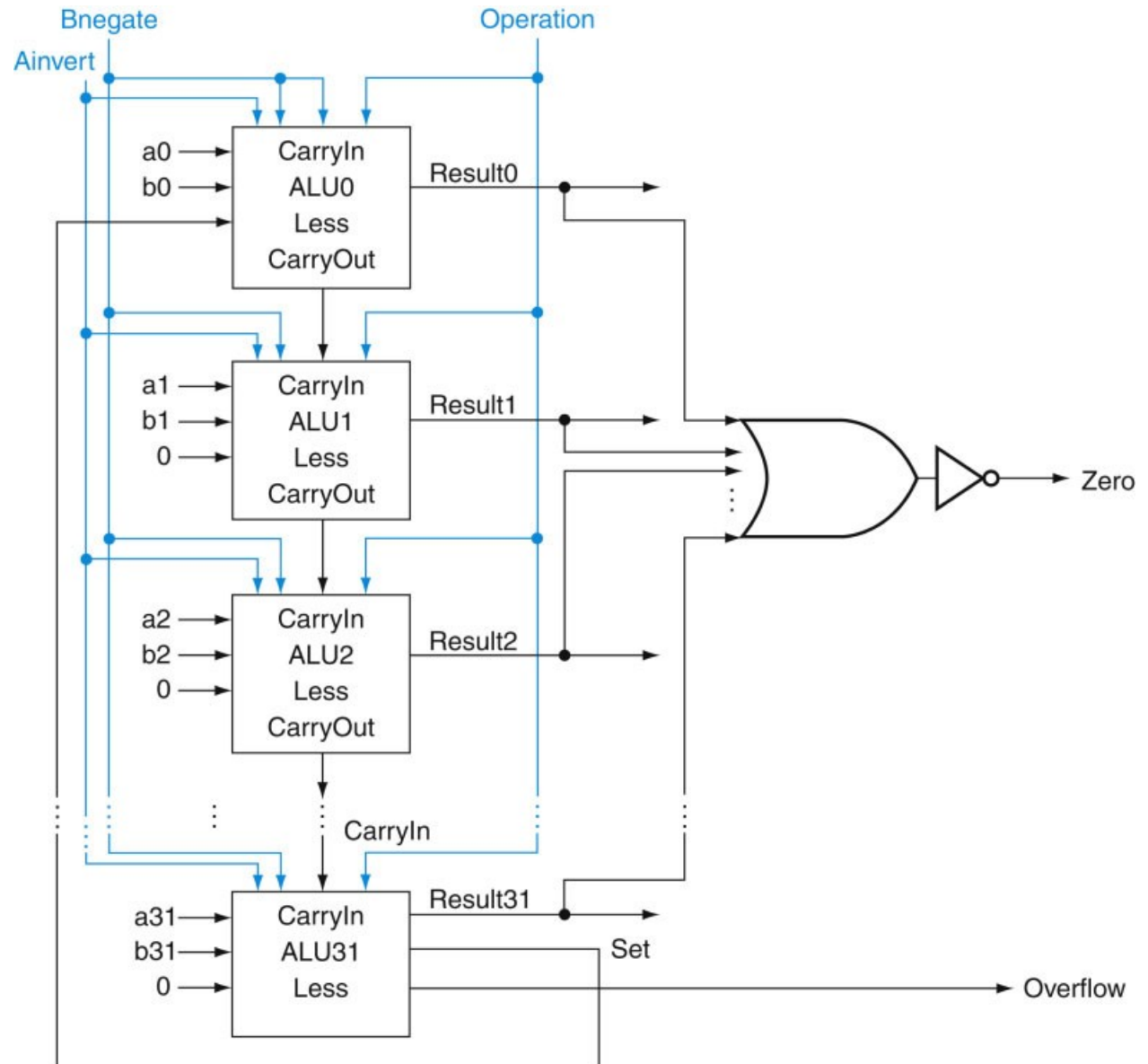
# Control Lines


What are the values of the control lines and what operations do they correspond to?



# Control Lines

What are the values of the control lines and what operations do they correspond to?

	Ai	Bn	Op
AND	0	0	00
OR	0	0	01
Add	0	0	10
Sub	0	1	10
SLT	0	1	11
NOR	1	1	00

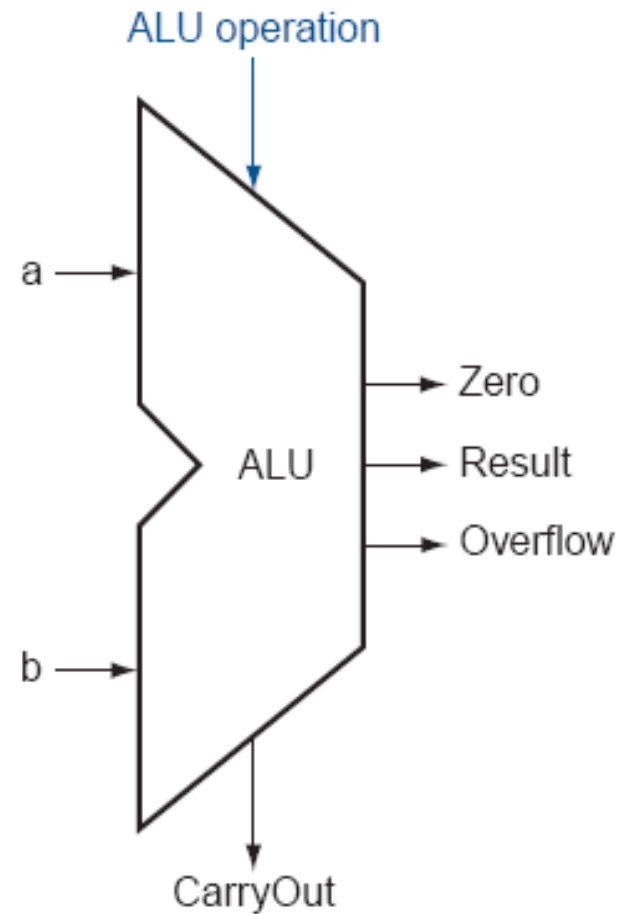

# Speed of Ripple Carry


- The carry propagates thru every 1-bit box: each 1-bit box sequentially implements AND and OR – total delay is the time to go through 64 gates!
- We've already seen that any logic equation can be expressed as the sum of products – so it should be possible to compute the result by going through only 2 gates!
- Caveat: need many parallel gates and each gate may have a very large number of inputs – it is difficult to efficiently build such large gates, so we'll find a compromise:
  - moderate number of gates
  - moderate number of inputs to each gate
  - moderate number of sequential gates traversed

# Clocks

- A microprocessor is composed of many different circuits that are operating simultaneously – if each circuit  $X$  takes in inputs at time  $TI_x$ , takes time  $TE_x$  to execute the logic, and produces outputs at time  $TO_x$ , imagine the complications in coordinating the tasks of every circuit
- A major school of thought (used in most processors built today): all circuits on the chip share a clock signal (a square wave) that tells every circuit when to accept inputs, how much time they have to execute the logic, and when they must produce outputs




# Clock Terminology

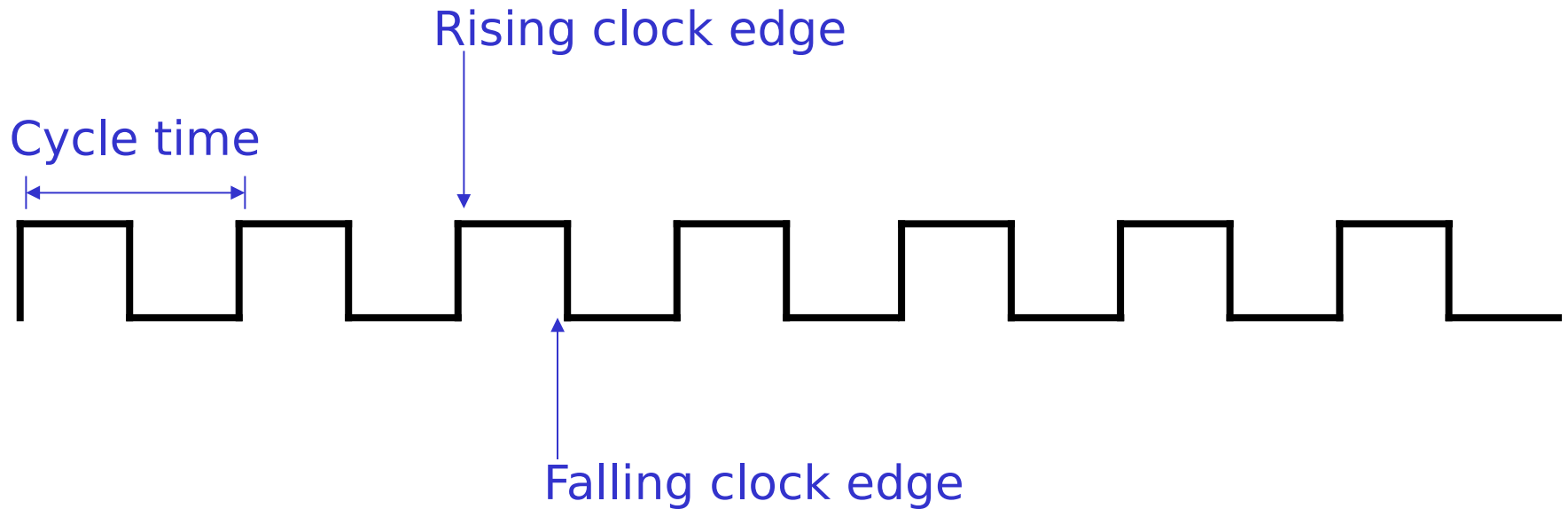


$$4 \text{ GHz} = \text{clock speed} = \frac{1}{\text{cycle time}} = \frac{1}{250 \text{ ps}}$$
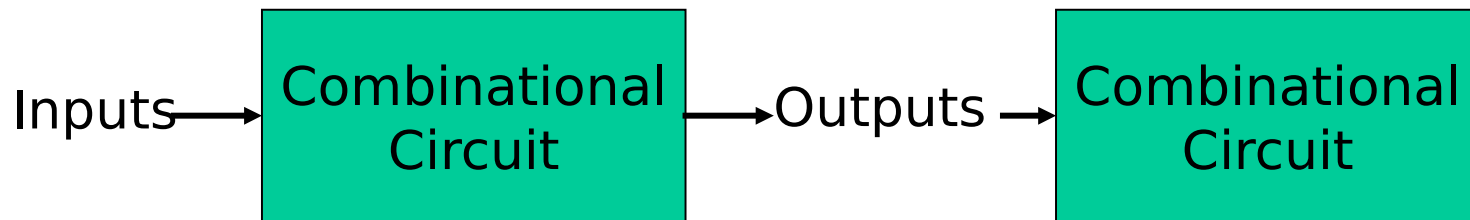
# Sequential Circuits

- Until now, circuits were combinational – when inputs change, the outputs change after a while (time = logic delay thru circuit)



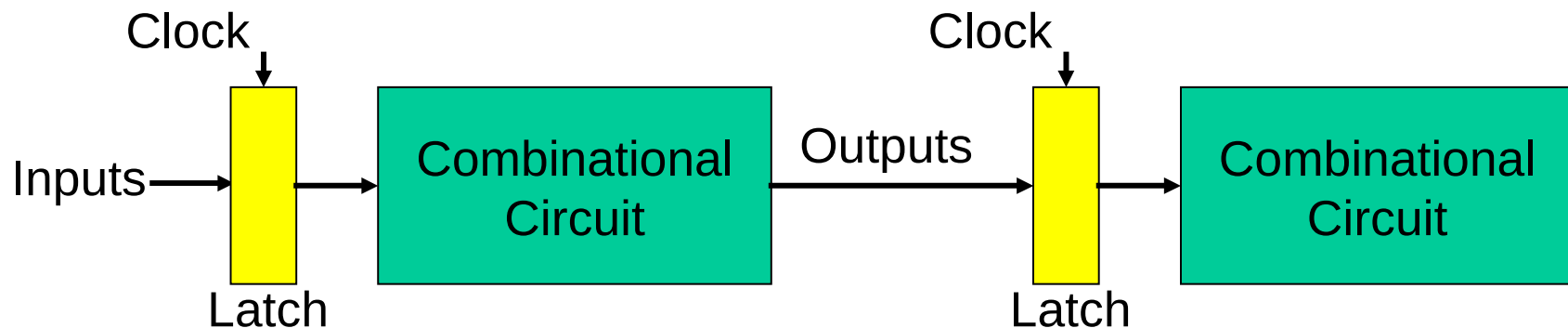- We want the clock to act like a start and stop signal – a “latch” is a storage device that separates these circuits – it ensures that the inputs to the circuit do not change during a clock cycle




Thank you!


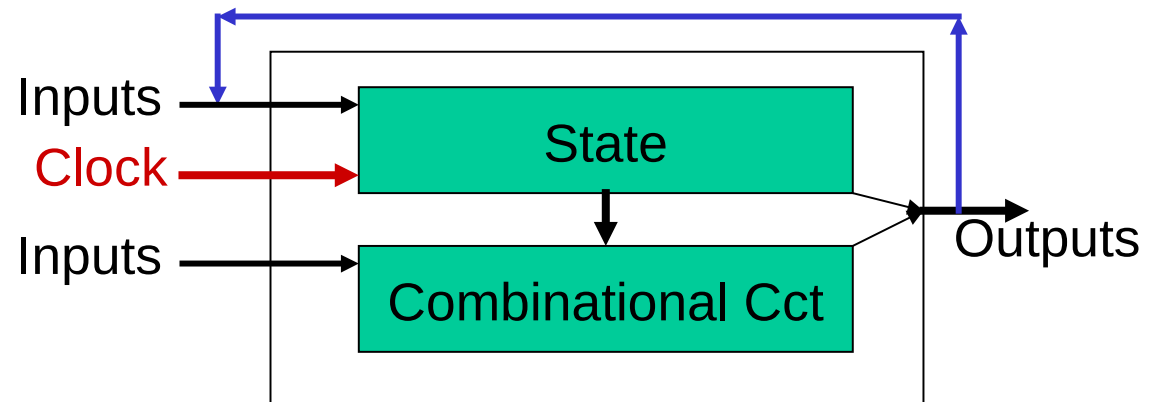
# Sequential Circuits

- Sequential circuit: consists of combinational circuit and a storage element
- At the start of the clock cycle, the rising edge causes the “state” storage to store some input values




- This state will not change for an entire cycle (until next rising edge)
- The combinational circuit has some time to accept the value of “state” and “inputs” and produce “outputs”
- Some of the outputs (for example, the value of next “state”) may feed back (but through the latch so they’re only seen in the next cycle)

# Sequential circuits

# Designing a Latch


- An S-R latch: set-reset latch
  - When Set is high, a 1 is stored
  - When Reset is high, a 0 is stored
  - When both are low, the previous state is preserved (hence, known as a storage or memory element)
  - Both are high – this set of inputs is not allowed

Verify the above behavior!

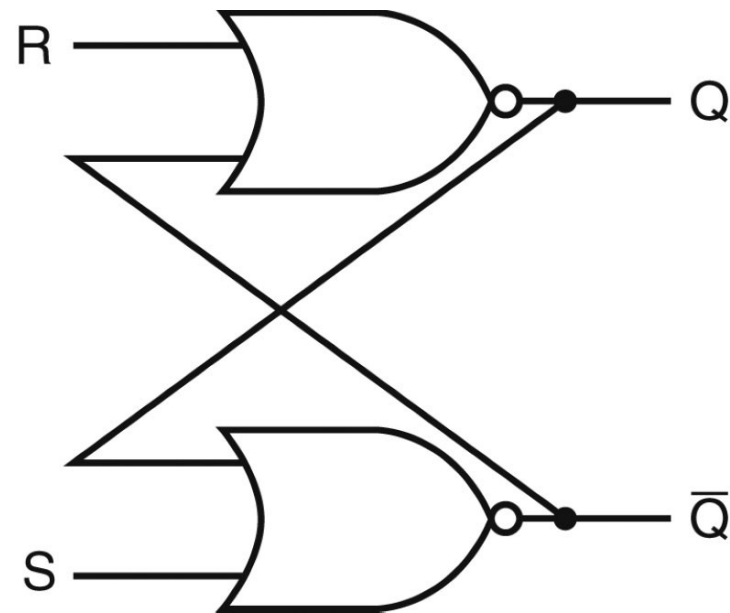

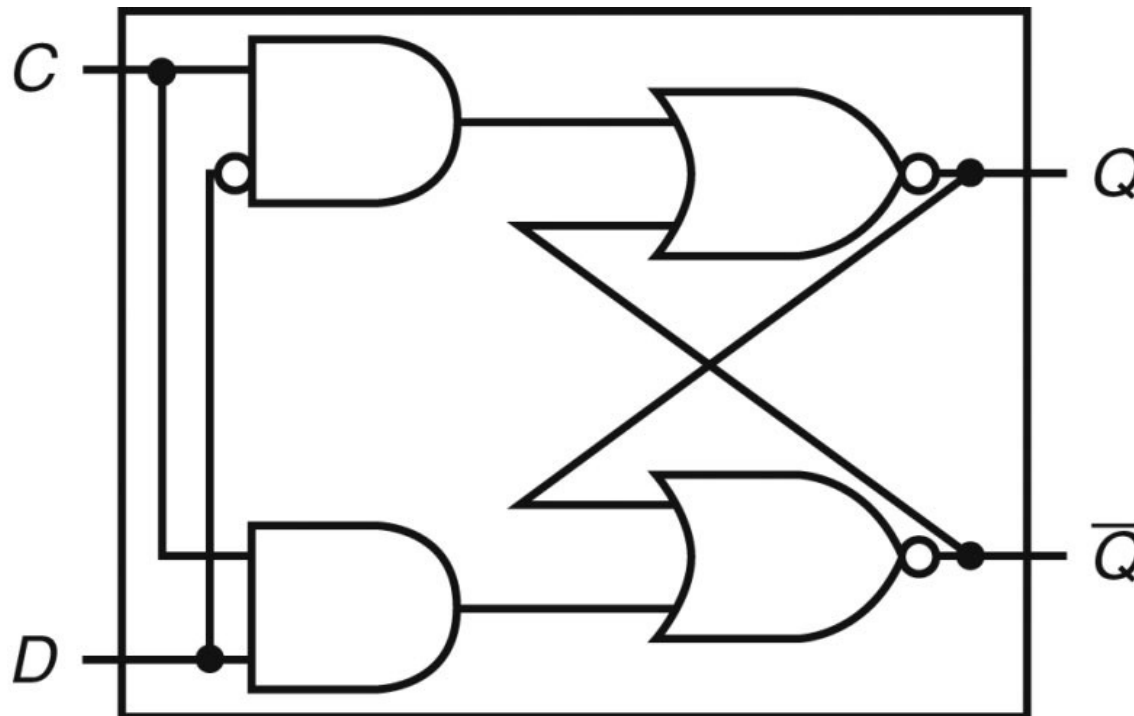
# D Latch

- Incorporates a clock
- The value of the input  $D$  signal (data) is stored only when the clock is high – the previous state is preserved when the clock is low



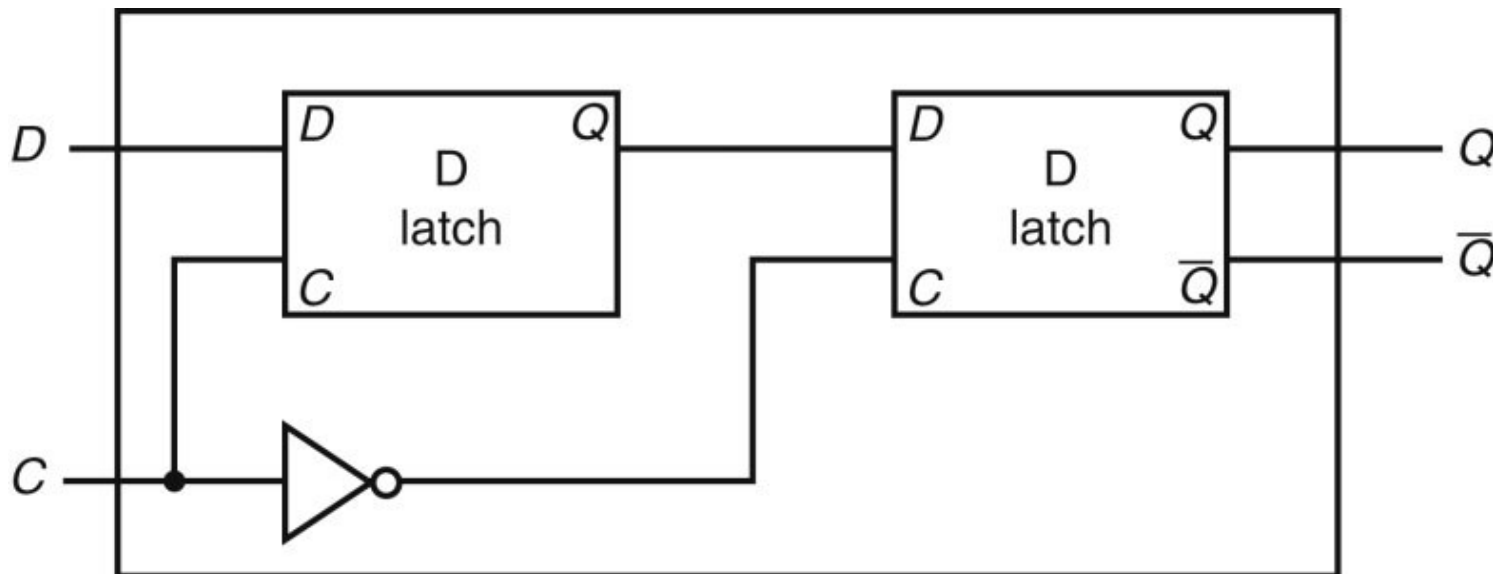
# D Flip Flop

- Terminology:  
Latch: outputs can change any time the clock is high (asserted)  
Flip flop: outputs can change only on a clock edge
- Two D latches in series – ensures that a value is stored only on the falling edge of the clock



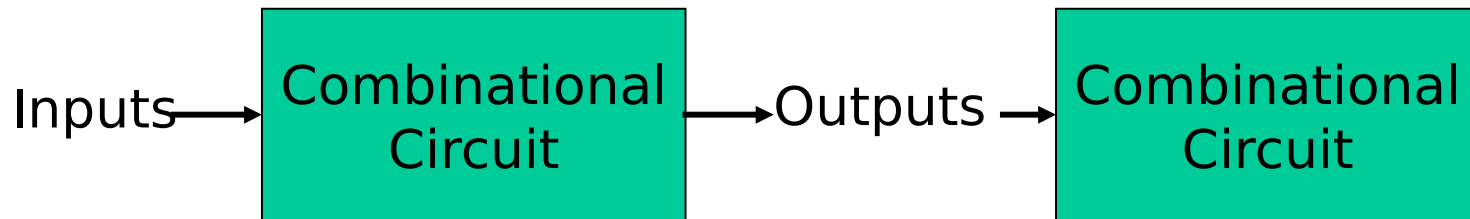
# Sequential Circuits

- Until now, circuits were combinational – when inputs change, the outputs change after a while (time = logic delay thru circuit)



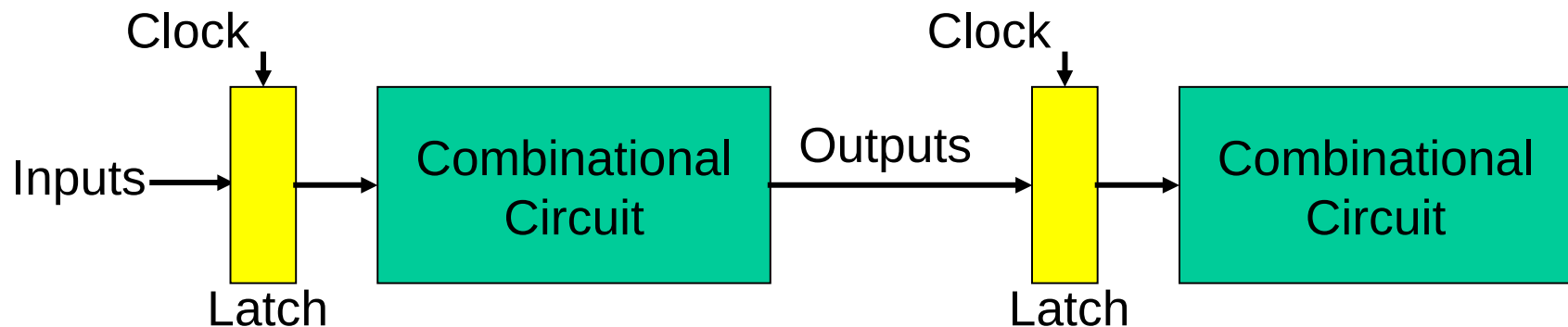
- We want the clock to act like a start and stop signal – a “latch” is a storage device that separates these circuits – it ensures that the inputs to the circuit do not change during a clock cycle



# Finite State Machines
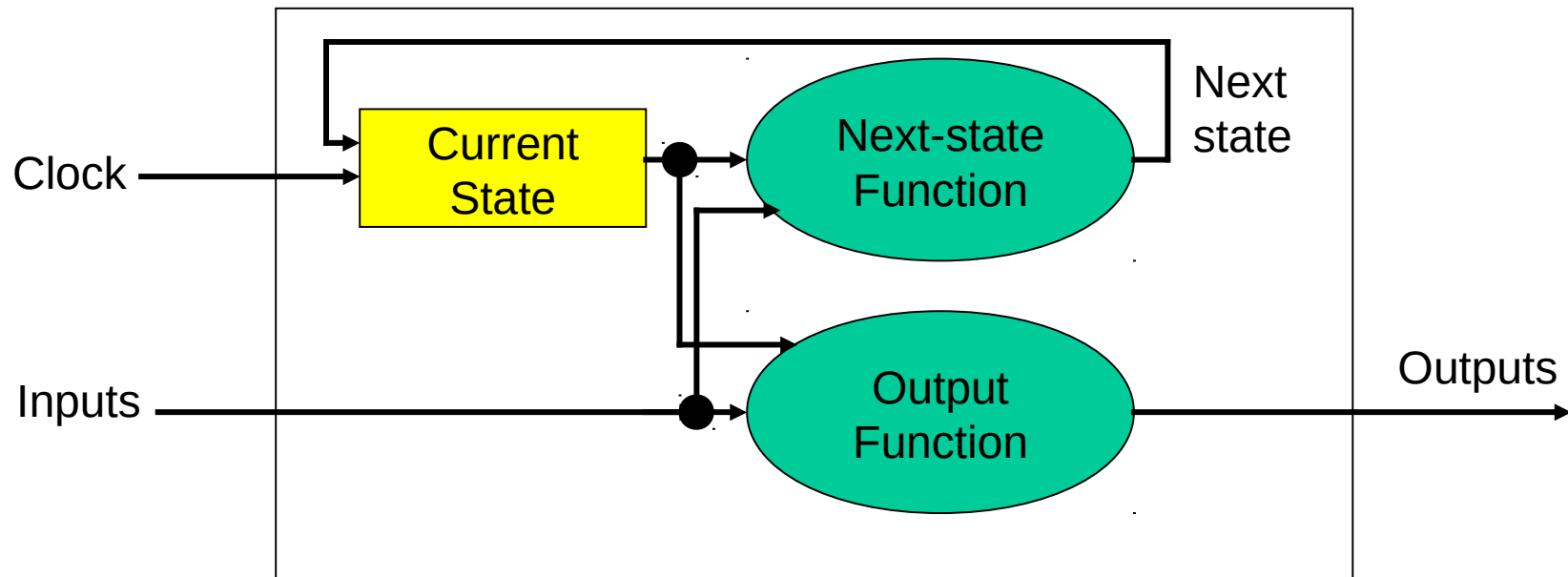
# Finite State Machine


- A sequential circuit is described by a variation of a truth table – a finite state diagram (hence, the circuit is also called a finite state machine)
- Note that state is updated only on a clock edge




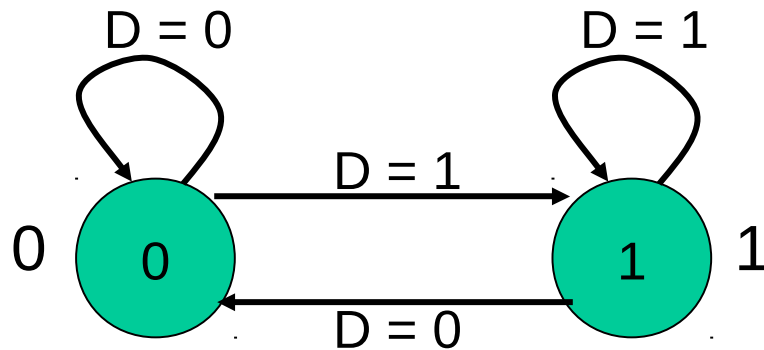
# State Diagrams

- Each state is shown with a circle, labeled with the state value – the contents of the circle are the outputs
- An arc represents a transition to a different state, with the inputs indicated on the label



This is a state diagram for \_\_\_\_?

# 3-Bit Counter

- Consider a circuit that stores a number and increments the value on every clock edge – on reaching the largest value, it starts again from 0

Draw the state diagram:

- How many states?
- How many inputs?

# 3-Bit Counter

- Consider a circuit that stores a number and increments the value on every clock edge – on reaching the largest value, it starts again from 0

Draw the state diagram:

- How many states?
- How many inputs?

